

31/07/2024 (16m)

QB ① * BINARY

CODES:

1) Binary to Gray code converter.

$$\begin{array}{r} 0001 \\ \downarrow \\ 0001 \end{array}$$

$$\begin{array}{l} 0+0=0 \\ 0+1=1 \\ 1+0=1 \\ 1+1=0 \end{array}$$

B ₃	B ₂	B ₁	B ₀	G ₃	G ₂	G ₁	G ₀
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	1	1	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	1	0
1	0	1	0	1	0	1	1
1	0	1	1	1	0	1	0
1	1	0	0	1	0	0	1
1	1	0	1	1	0	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	0

k-map G₁₀

$B_3 B_2 \backslash B_1 B_0$	00	01	11	10
00	0	1	0	1
01	0	1	0	1
11	0	1	0	1
10	0	1	0	1

$$= \bar{B}_1 B_0 + B_1 \bar{B}_0$$

$$G_{10} = B_1 \oplus B_0$$

G₁

$B_3 B_2 \backslash B_1 B_0$	00	01	11	10
00	0	0	1	1
01	1	1	0	0
11	1	1	0	0
10	0	0	1	1

$$= \bar{B}_2 B_1 + B_2 \bar{B}_1$$

$$G_{11} = B_2 \oplus B_1$$

G₂

$B_3 B_2 \backslash B_1 B_0$	00	01	11	10
00	0	0	0	0
01	1	1	1	1
11	0	0	0	0
10	1	1	1	1

$$\bar{B}_3 B_2 + B_3 \bar{B}_2$$


$$G_{12} = B_3 \oplus B_2$$

G₃

$B_3 B_2 \backslash B_1 B_0$	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	1	1	1	1
10	1	1	1	1

$$= B_3$$


$$G_{13} = B_3$$

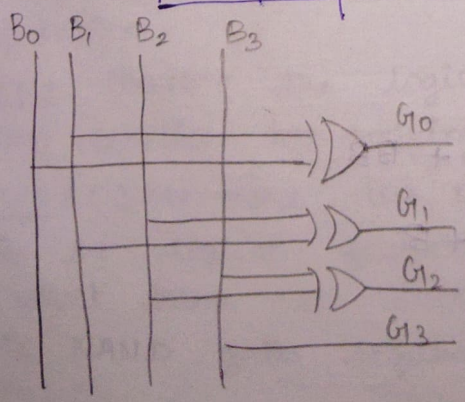


Logic gates.

② Q.B (16m)
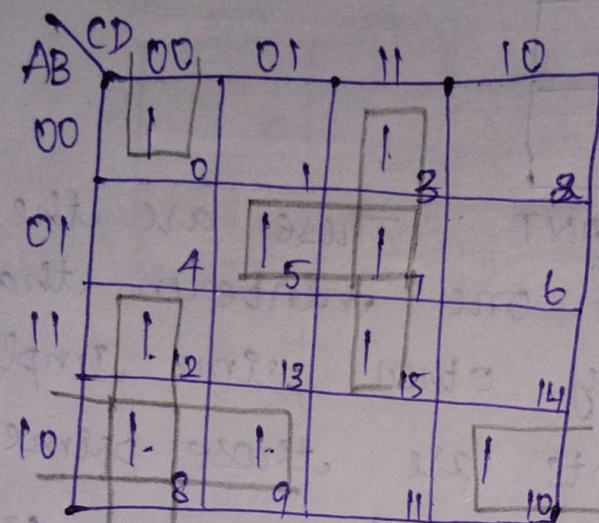
$$f(A, B, C, D) = \sum (0, 3, 5, 7, 8, 9, 10, 12, 15)$$


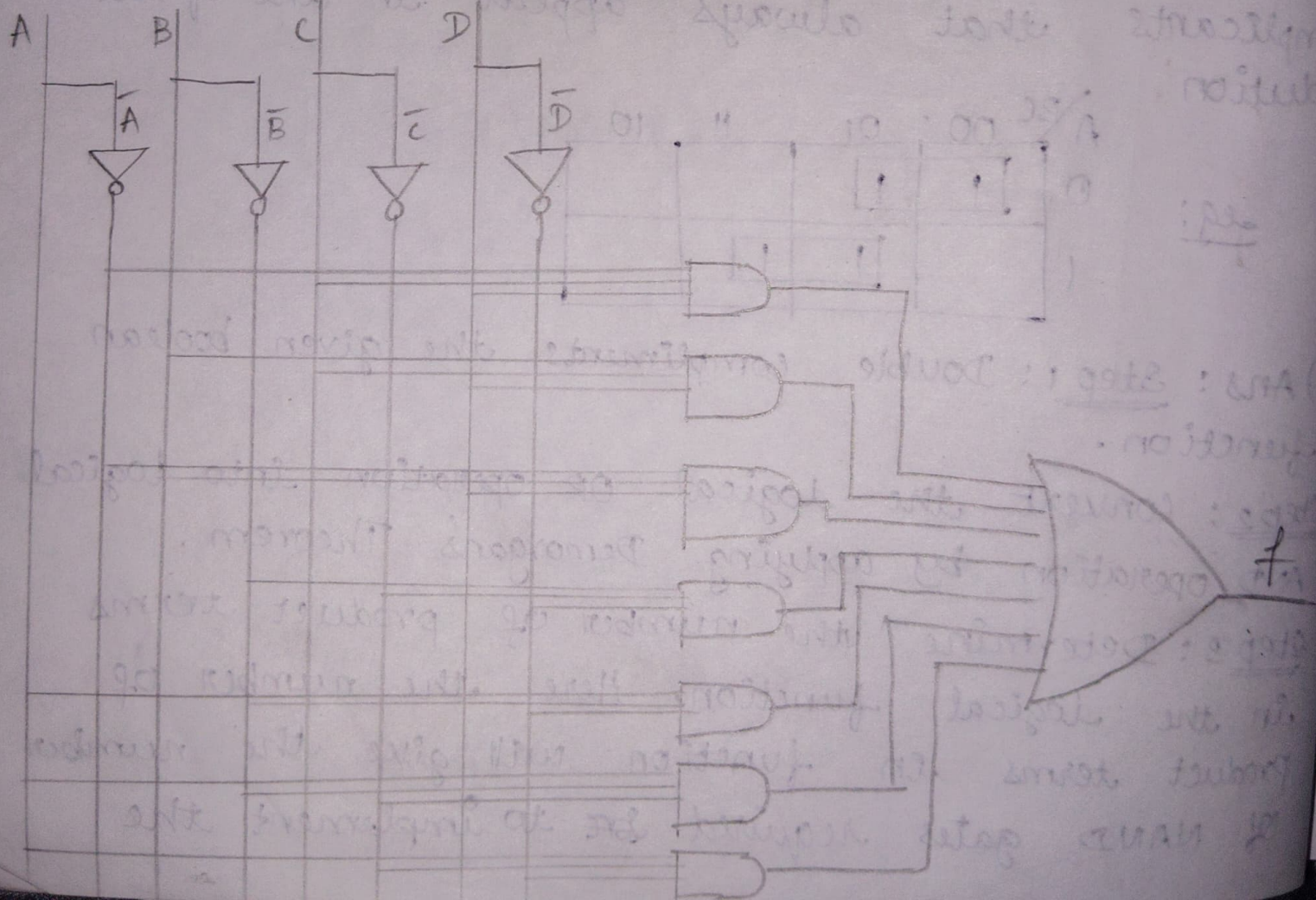
$$= \bar{A}CD + BCD + \bar{A}BD + \bar{B}\bar{C}\bar{D} + A\bar{B}\bar{D} + A\bar{B}\bar{C} + A\bar{C}\bar{D} //$$



2) Simplify the Boolean expression using k-map

$$Y = \bar{A}\bar{B}\bar{C}D + \bar{A}BC\bar{D} + AB\bar{C}D + A\bar{B}\bar{C}D + ABC\bar{D}$$

③

QB


(16m)

$$f = \sum (5, 6, 9, 13, 14)$$

AB \ CD	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

$$= \bar{B}\bar{C}D + A\bar{C}D +$$

$$BC\bar{D}$$

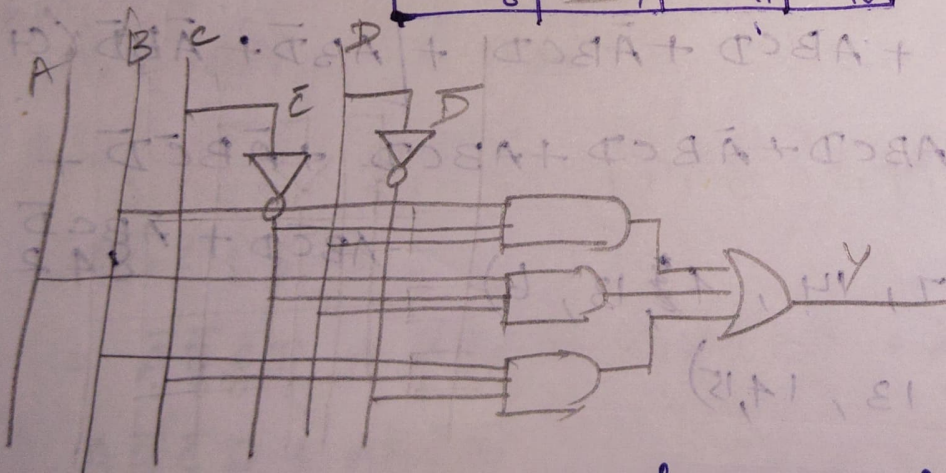

1) (3m) (4) Q.8.B
 2) Define prime implicant and essential prime implicant.

(10m) 11) Write the procedure for obtaining the logic diagram with NAND gates from a boolean expression

⇒ 1) Ans: A group of squares as rectangles made up of a bunch of adjacent minterms which is allowed by the definition of k-map are called prime implicant, that is all possible groups formed in k-map.

eg:

A \ BC	00	01	11	10
0	1	1		
1		1	1	

ESSENTIAL PRIME IMPLICANT: These are the groups that cover atleast one minterm that cannot be covered by any other prime implicant. Essential prime implicants are those prime implicants that always appear in the final solution

eg:

A \ BC	00	01	11	10
0	1	1		
1		1	1	

ii) Ans: Step 1: Double complements the given boolean function.

Step 2: Convert the logical OR operation into logical AND operation by applying Demorgan's Theorem.

Step 3: Determine the number of product terms in the logical function. Here the number of product terms in function will give the number of NAND gates required to implement the


function.

Step 4: Finally implement the logic circuit diagram by connecting all the NAND gates together according to logic expression.

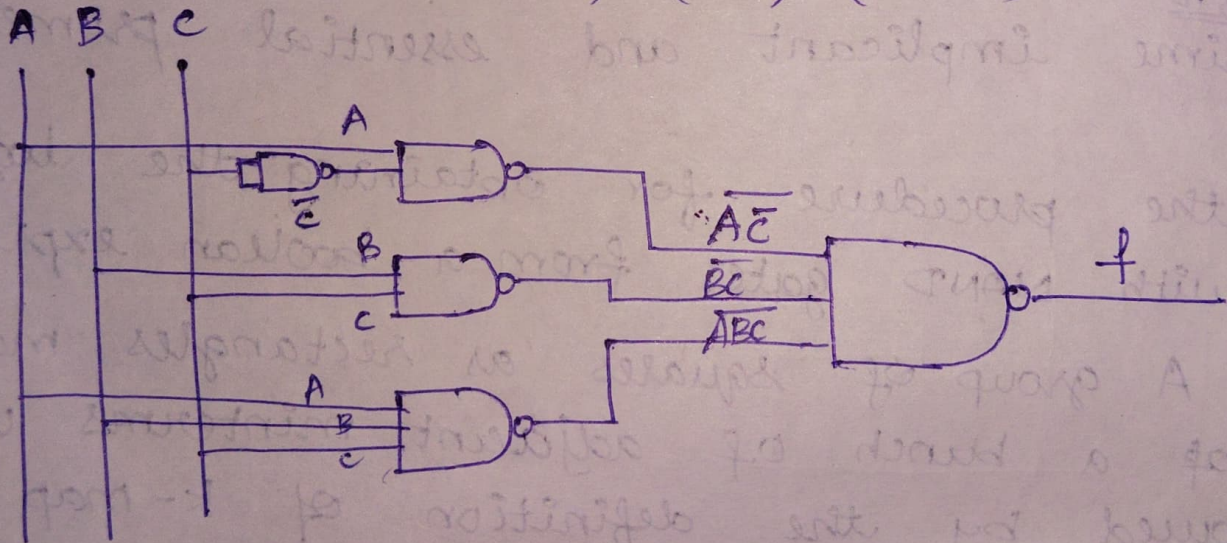Example:

$$f = A\bar{C} + BC + ABC$$

$$\begin{aligned}\bar{f} &= \overline{f} = \overline{A\bar{C} + BC + ABC} \\ &= (\overline{A\bar{C}}) \cdot (\overline{BC}) \cdot (\overline{ABC})\end{aligned}$$



2) Construct the switching function $f(x, y, z) = \sum m(1, 2, 3, 4, 5, 7)$ using k-map.


(1m)

(A)

Q.B

$x \backslash yz$	00	01	11	10
0	0	1	1	1
1	1	1	1	0

$$= \cancel{x}z + x\bar{y} + \bar{x}y$$

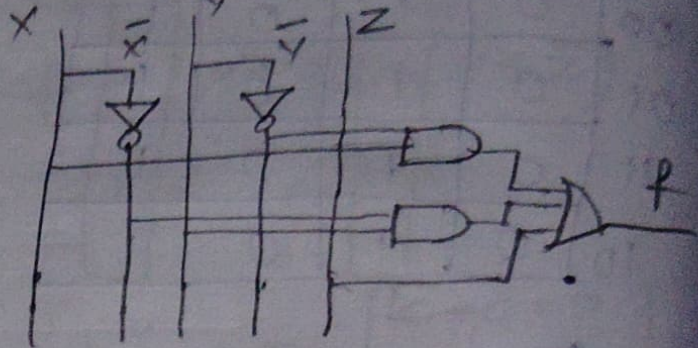

⑤ Q.B (16m)

7) Solve the boolean function using k-map in SOP and POS $f(w, x, y, z) = \sum (1, 3, 4, 6, 9, 11, 12, 14)$


SOP \Rightarrow

Wx \ yz	00	01	11	10
00	0	1	1	2
01	1	4	5	7
11	1	12	13	15
10	8	1	1	10

$$= x\bar{z} + \bar{x}z$$

$$f(w, x, y, z) = \pi (0, 2, 5, 7, 8, 10, 13, 15)$$

(logic gates)

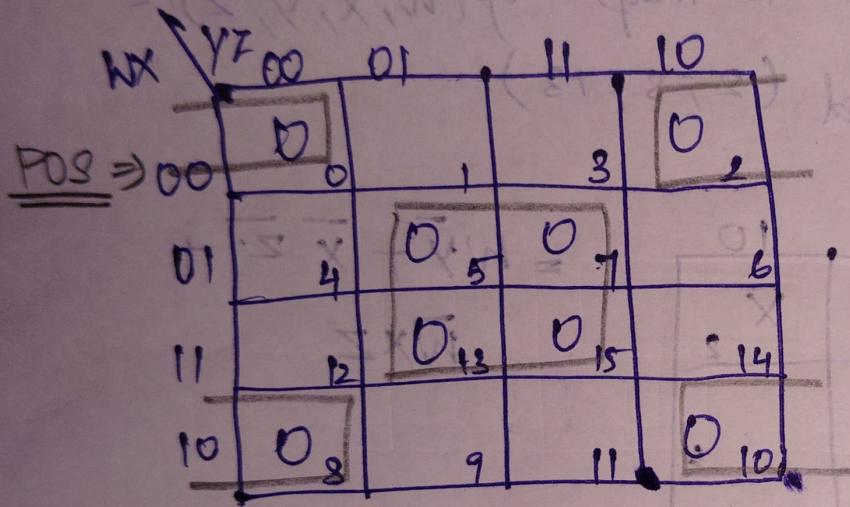

$$= \overline{XZ}$$

$$f = (x + z) \cdot (\bar{x} + \bar{z})$$

("logic" gates)

$$0 + 0 = 0$$


5) Reduce the function using k-map $f(w, x, y, z) = \sum_m (0, 7, 8, 9, 10, 12) + \sum_d (2, 5, 13)$

(18m)

Q.B

w \ yz	00	01	11	10
00	1			X
01		X	1	
11	1	X		
10	1			1
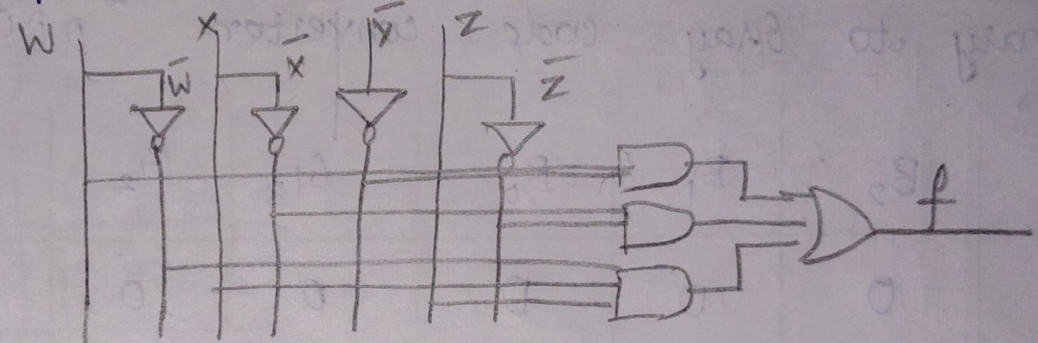
$$= W\bar{Y} + \bar{X}\bar{Z} + \bar{W}XZ$$




(8m) Q.B


b) Reduce the function using k-map. $f(a, b, c) = \sum_m (0, 1, 3, 7) + \sum_d (2, 5)$

a \ bc	00	01	11	10
0	1	1	1	X
1		X	1	

$$= C + \bar{A}$$

$$= \bar{A} + C$$

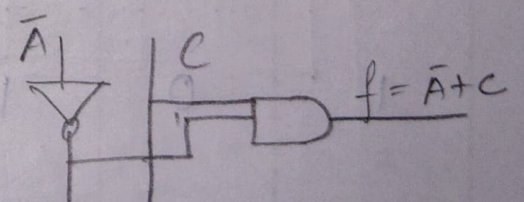

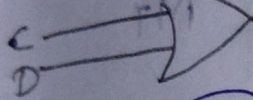

De - Morgan's Theorem : (8m) ⑦ Q.B

$$1) \overline{A+B} = \bar{A} \cdot \bar{B}$$

A	B	A+B	$\overline{A+B}$	\bar{A}	\bar{B}	$\bar{A} \cdot \bar{B}$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

$$\overline{A+B} = \overline{A} \cdot \overline{B}$$

\therefore Hence proved.

$$2) \overline{A \cdot B} = \overline{A} + \overline{B}$$

A	B	$A \cdot B$	$\overline{A \cdot B}$	\overline{A}	\overline{B}	$\overline{A} + \overline{B}$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

\therefore Hence proved.

3) Express $x + yz$ as the sum of minterms:

(8m)

Ⓢ.B

$$f = x(y + \bar{y})(z + \bar{z}) + yz(x + \bar{x})$$

$$f = (xy + x\bar{y})(z + \bar{z}) + xyz + \bar{x}yz$$

$$f = xyz + xy\bar{z} + x\bar{y}z + x\bar{y}\bar{z} + xyz + \bar{x}yz$$

$$f = \sum (7, 6, 5, 4, 7, 3)$$

$$f = \sum_m (3, 4, 5, 6, 7)$$

(8 mark)

421

1108124

(4m)

Q.B (8)

Find the octal equivalent of hexa decimal numbers

AB.CD

¹⁰ ¹¹ ¹² ¹³
A B . C D

010 101011 . 110011010

(253.632)₈

8 4 2 1
1 0 1 1
1 0 1 0
1 1 0 0
1 1 0 1

4) Simplify : (4m) Q.B (8)

$$i) Y = AB'D + AB'D'$$

$$ii) Z = (A' + B)(A + B)$$

$$i) Y = AB'D + AB'D'$$

$$= AB'(D + D')$$

$$= AB'$$

$$ii) Z = (A' + B)(A + B)$$

$$= A'A + A'B + AB + BB$$

$$= 0 + A'B + AB + B$$

$$= B(A' + A) + B$$

$$= B + B = B //$$

	01	11	10	00	
01	0	0	0	0	00
11	0	0	0	0	10
10	1	1	1	1	11
00	1	1	1	1	01